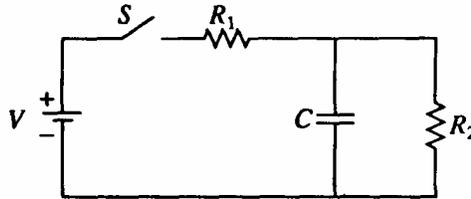



AP Physics C Review 17 Capacitors

1. A 10 nF parallel-plate capacitor holds a charge of $50 \mu\text{C}$ on each plate.
 - a. What is the potential difference between the plates?
 - b. If a distance of 0.2 mm separates the plates, what is the area of each plate?




In the circuit shown above, the battery supplies a constant voltage V when the switch S is closed. The value of the capacitance is C , and the value of the resistances are R_1 and R_2 .

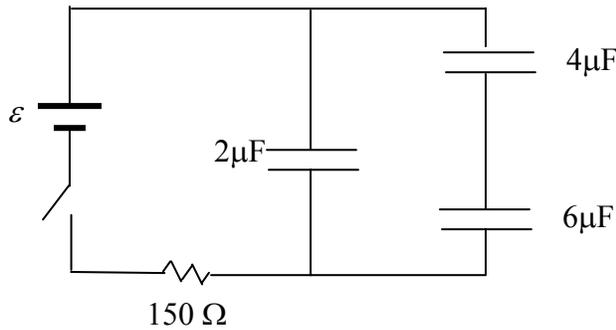2. Immediately after the switch is closed, the current supplied by the battery is
 - A) $V/(R_1 + R_2)$
 - B) V/R_1
 - C) V/R_2
 - D) $V(R_1 + R_2)/R_1R_2$
 - E) zero
3. A long time after the switch has been closed, the current supplied by the battery is
 - A) $V/(R_1 + R_2)$
 - B) V/R_1
 - C) V/R_2
 - D) $V(R_1 + R_2)/R_1R_2$
 - E) zero
4. a) Find the equivalent capacitance for the circuit.



- b) If $\varepsilon = 6 \text{ V}$ and the switch is closed, what is the current through the resistor?
- c) If the switch is closed for a while, find the charge on each capacitor.

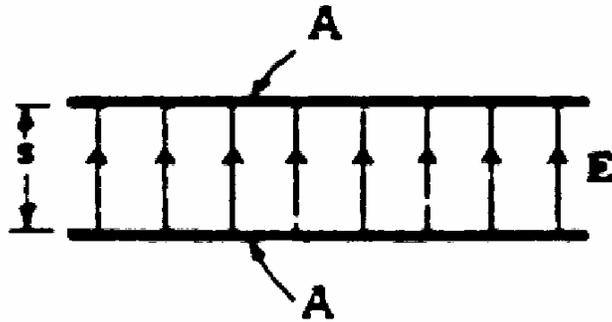
3. A uniform electric field E is established between two capacitor plates, each of area A , which are separated by a distance s as shown below.



- (a) What is the electric potential difference V between the plates?
- (b) Specify the sign of the charge on each plate.

The capacitor shown is then connected electrically through a resistor to a second parallel-plate capacitor, initially uncharged, whose plates have the same area A but a separation of only $s/2$.

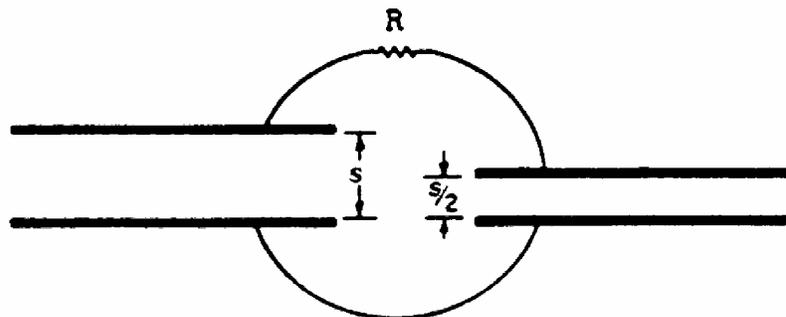- (c) Indicate on the diagram below the direction of the current in each wire, and explain why the current will eventually cease.



- (d) After the current has ceased, which capacitor has the greater charge? Explain your reasoning.
- (e) The total energy stored in the two capacitors after the current has ceased is less than the initial stored energy. Explain qualitatively what has become of this "lost" energy.